

CMOS Logic Circuit Design

<http://www.rcns.hiroshima-u.ac.jp>

Link(リンク): センター教官講義ノート の下 CMOS論理回路設計

Special-Purpose Digital Circuits

- Buffer Circuits
- Path-Selector Circuits
- Information-Storing Circuits
- Trigger Circuits
- Multi-Vibrator Circuits
- Voltage-Generator Circuits

Necessary Functions other than Logic Operations

- 1) Transmission of signals over long interconnection lines or to many receivers
 - Buffer (inverting, non-inverting, tri-state)
- 2) Selection of an interconnection for a Signal according to a condition
 - Selector (multiplexer, demultiplexer)
- 3) Storing an information for some time
 - Flip-flop, latch
- 4) Removing Noise from a Signal
 - Trigger circuits
- 5) Generation of Synchronous or Asynchronous Control Signal
 - Multi-vibrator circuits (a-stable, bi-stable, mono-stable)
- 6) Generation of other Voltages than VDD or VSS
 - Voltage generator circuits


CMOS logic circuits do contain more than only logic gates.

Buffer Circuits

- Increasing the driving capability of a logic signal for large load capacities
- Conventional non-inverting buffers
- Inverting buffers
- Tri-state buffers

Reduction of Logic-Gate Fan-Out with a Buffer

NAND-gate with fan-out = k, fan-in = m

 


Delay without buffer

$$t_{df,NAND} = m \cdot (m \cdot t_{fin} + k \cdot t_{fex})$$

$$t_{dr,NAND} = m \cdot t_{rin} + k \cdot t_{rex}$$

NAND-gate with fan-out = 1, fan-in = m

 

Non-inverting Buffer




Delay with buffer

$$t_{df,NAND} = m \cdot (m \cdot t_{fin} + t_{fex}) + t_{buffer}$$

$$t_{dr,NAND} = m \cdot t_{rin} + t_{rex} + t_{buffer}$$

The delay of a circuit with large fan-out (i. e. large output load) can be reduced with a buffer, if $(k-1) \cdot t_{rex} > t_{buffer}$ is valid.

   Construction of Non-Inverting CMOS Buffers



Optimum choice of A and N




$$A_{ni-buffer} = \left[\frac{C_{load}}{C_{in1}} \right]^{\frac{1}{2N}}$$

$$N_{ni-buffer} = \text{int} \left[\frac{1}{2} \ln \frac{C_{load}}{C_{in1}} \right]$$

(C_{in1} is the input capacity of the 1st inverter)

Non-inverting buffers have even number of inverters. Each stage has a factor $A_{ni-buffer}$ (C_{load}, C_{in}) larger driving capability.

Construction of Inverting CMOS Buffers

   

Optimum Choice of A and N

$$A_{i\text{-buffer}} = \left[\frac{C_{\text{load}}}{C_{\text{in1}}} \right]^{\frac{1}{2N+1}}$$


$$N_{i\text{-buffer}} = \text{int} \left[\frac{1}{2} \ln \left(\frac{C_{\text{load}}}{C_{\text{in1}}} \right) - \frac{1}{2} \right]$$

(C_{in1} is the input capacity of the 1st inverter)

Inverting buffers use an odd number of cascaded inverters. Each stage has again $A_{i\text{-buffer}}(C_{\text{load}}, C_{\text{in}})$ larger driving capability.

Tri-State Inverter


Symbol

 

Truth Table

En	In	Out
0	0	floating
0	1	floating
1	0	1
1	1	0


CMOS-Circuit Implementation

 



A tri-state inverter has an additional high-impedance or floating output state selected with an enable signal. It can be built with a conventional inverter and a transmission gate.

Tri-State Buffers


**non-inverting
tri-state buffer**

 

**inverting
tri-state buffer**

  

CMOS-Circuit Implementation

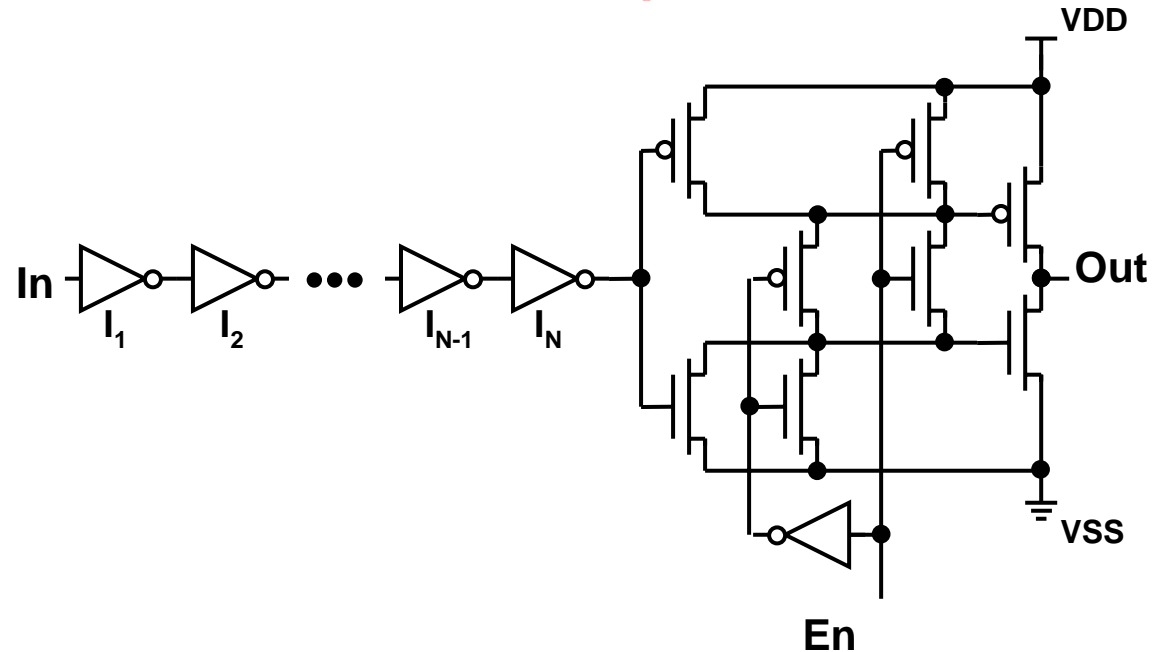


A tri-state buffer combines high driving capability for a large load capacity C_{load} and the possibility of a floating output.

Path-Selector Circuits

- Multiplexer- and Demultiplexer Principles
- Implementation with Transmission Gates
- Series Connection of Transmission Gates
- Implementation with Tri-State Inverters or Tri-State Buffers

Multiplexer and Demultiplexer Principles

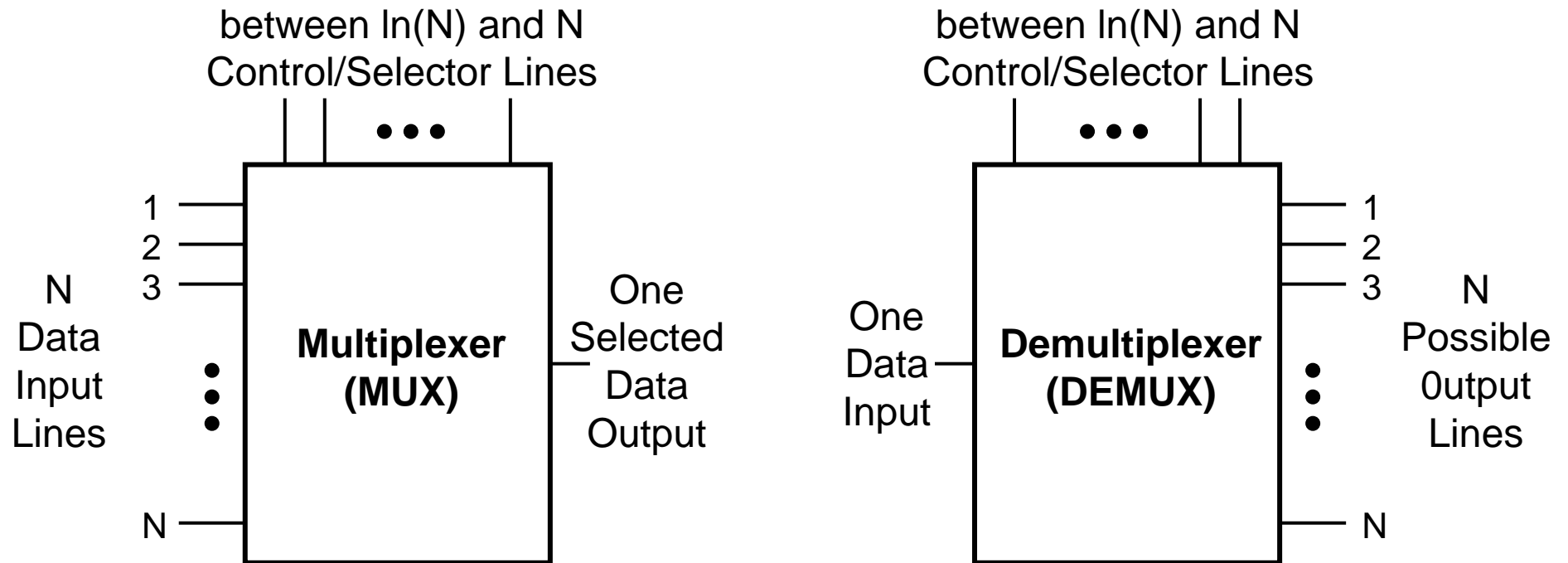

Conditional signal-path selection is performed with multiplexer- or demultiplexer circuits.


Multiplexer Realization with Transmission Gates

Transmission Gates

Symbols




Circuits

 


4-Input Multiplexer

Minimum Transmission Gates

 


Minimum Select Signals

 


Path-selector realization is easiest by transmission gates.

Series Connection of Transmission Gates

 Series of N transmission gates driving a load



 Delay model for a series of N transmission gates




Delay equation as a function of N transmission gates

$$t_{PS,hl} \approx t_{PS,lh} \approx (R_n \parallel R_p)(C_{load}) \cdot N + 0.35 \cdot (R_n \parallel R_p)(C_{inn} + C_{inp}) \cdot N^2$$


A series connection of N transmission gates represents an RC-chain. Therefore, its delay time increases with N^2 .

MUX/DEMUX Realization with Tri-State Buffers

Multiplexer

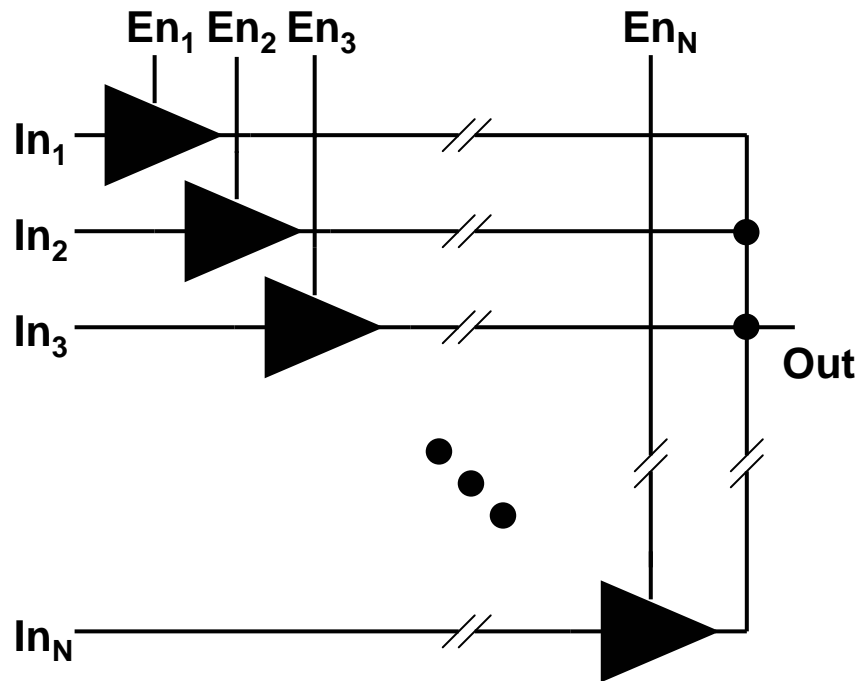

Demultiplexer

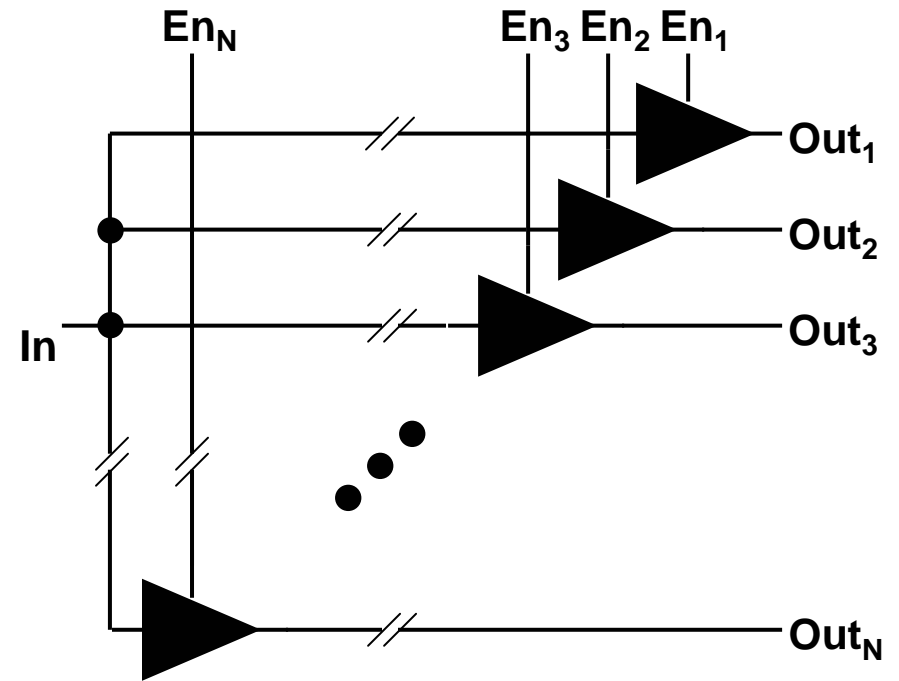


With tri-state buffers the delay problem of signal-path selectors is solved at the cost of larger integration-area.

Information-Storing Circuits

- Stabilizing-Feedback Principle
- Set-Reset Flip-Flop
- Clocked Flip-Flops
 - Level Sensitive Flip-Flops
 - Edge-Triggered Flip-Flops
 - Flip-Flop Timing

Stabilizing-Feedback Principle of Data Storage

Stabilizing inverter-feedback coupling

 


Resulting stable circuit states

Stable States	Q	\bar{Q}
“one”	1	0
“zero”	0	1


By feeding back the identical signal to a circuit node, stable circuit states result, which are usable for data storage.

Set-Reset (SR) Flip-Flop

 Circuit diagram
(constructed with NAND gates)



Logic Symbol

 


Truth table

S	R	Q	\bar{Q}
0	0	1	1
1	0	1	0
0	1	0	1
1	1	Q	\bar{Q}


Set-reset flip-flops extend the stabilizing feedback principle by a method for external modification of the stored data.

Level-Sensitive Data (D) Flip-Flop

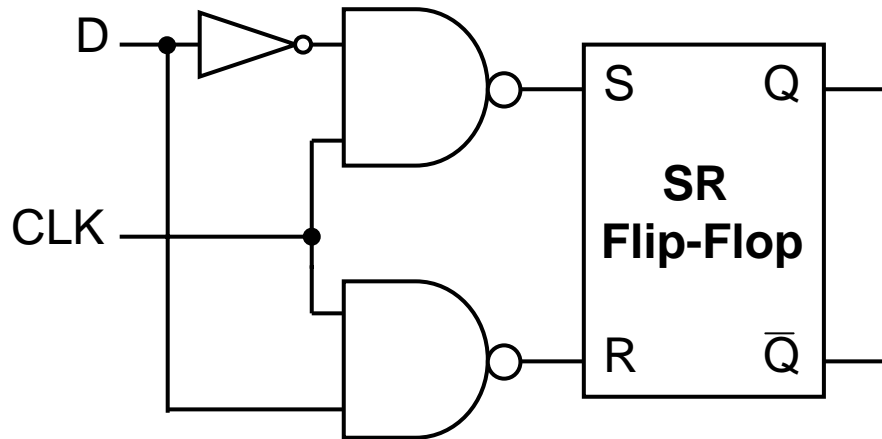Circuit diagram
(constructed with NAND gates)




Logic Symbol

 

The level-sensitive data (D) flip-flop extends the SR flip-flop with additional circuitry for clock-controlled writing of data.

Latch: Transmission-Gate Version of D Flip-Flop

 
Circuit diagram of a latch
(data flip-flop constructed with inverters and transmission gates)



The simplest construction of level-sensitive data (D) flip-flops has 2 inverters and 2 transmission gates and is called “latch”.


Edge-Triggered data (D) Flip-Flop

 Circuit diagram of a D flip-flop into which data is written at the positive edge (low-high) change of the clock (constructed with 2 latches)



The edge-triggered D flip-flop has 2 latches. Data transfer to the slave latch occurs only at transition edges of the clock.

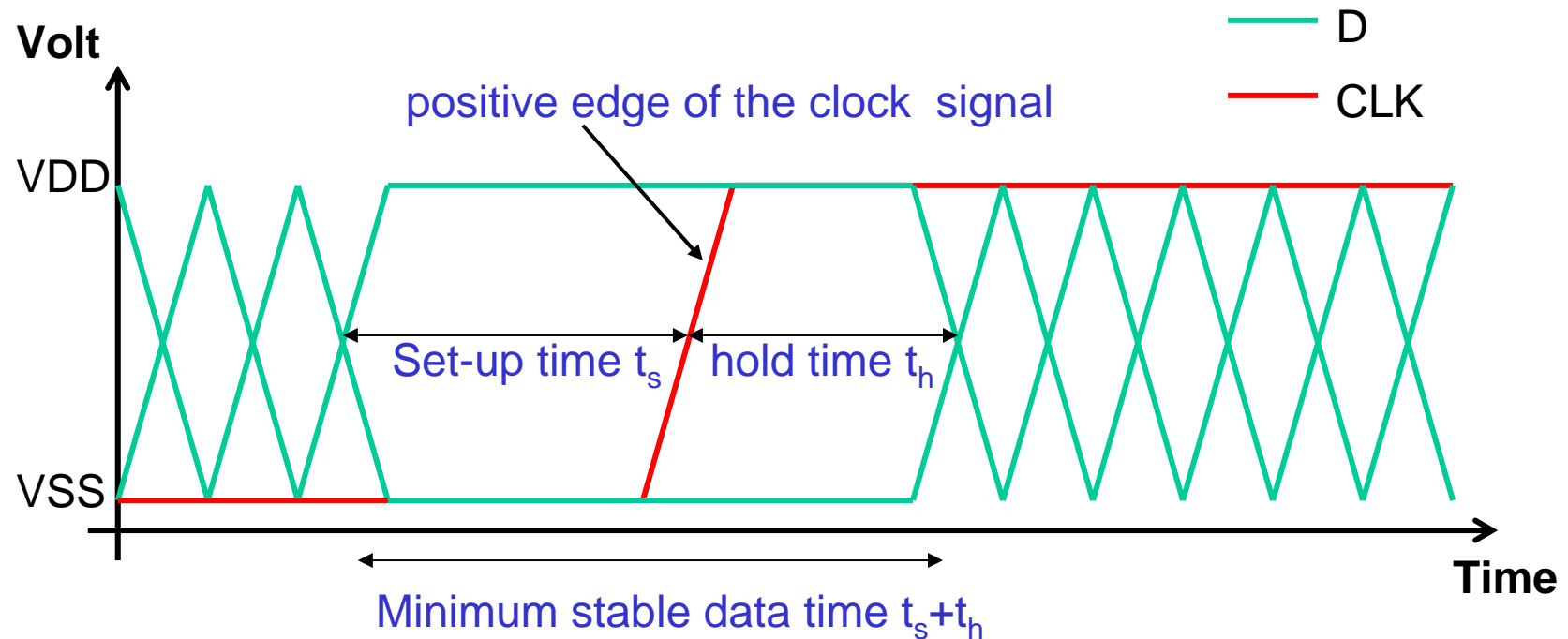Timing of Flip-Flops for Safe Data Writing




The safe operation of a flip-flop requires stable data signals for a minimum time around the clock edge, which determines data transfer into the storage part of the flip-flop.


Trigger Circuits

- Removal Possibilities of Signal Noise
- Schmitt-Trigger Circuit

Signal Noise and Removal Possibilities

 

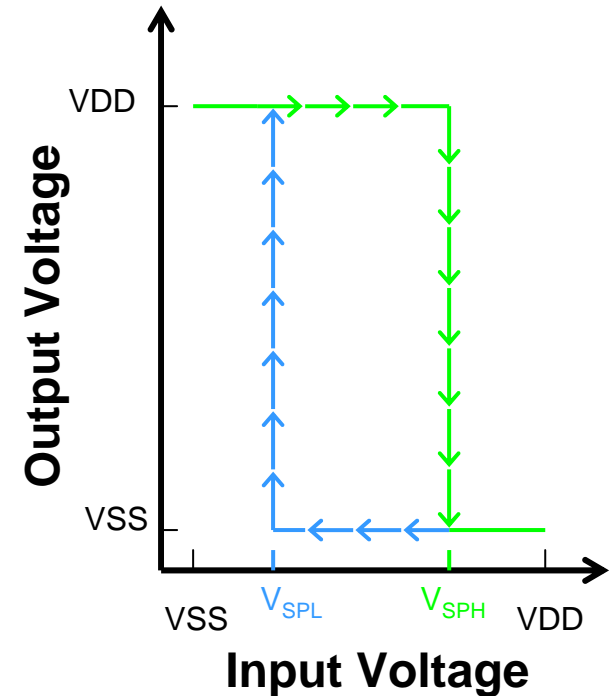
Desired Switching-Point Characteristic of Circuit



Noise can be removed from a signal with a circuit who has different switching points for low-high and high-low transition.

Schmitt-Trigger Circuit


Schmitt-Trigger Symbol

 

Design of n-MOS Transistors M1 and M2 determines the High-Switching Point

$$\frac{\beta_1}{\beta_2} \approx \left[\frac{VDD - V_{SPH}}{VSS + V_{SPH} - V_{TH,n}} \right]^2$$

CMOS Circuit

 

Design of p-MOS Transistors M5 and M6 determines the Low-Switching Point

$$\frac{\beta_5}{\beta_6} \approx \left[\frac{VSS + V_{SPL}}{VDD - V_{SPL} - V_{TH,p}} \right]^2$$


The CMOS inverter circuit can be easily modified to obtain an inverting Schmitt-trigger circuit to reduce input-signal noise.

Multi-Vibrator Circuits


- Destabilizing-Feedback Principle
- A-Stable Multi-Vibrator or Oscillator
- Bi-Stable Multi-Vibrator or Flip-Flop
(see Part on Information-Storing Circuits)
- Mono-Stable Multi-Vibrator

Destabilizing Feedback: Oscillator Circuits

Destabilizing inverter-feedback coupling

 

 
Resulting unstable (oscillating) signals at circuit nodes



By feeding back the inverted signal to a circuit node, an unstable state occurs, which is used for oscillator circuits.

Ring-Oscillator Circuit with N Stages

 Ring-Oscillator constructed with an odd number N of inverters



Obtained oscillator frequency


$$f_{osc} \approx \frac{1}{N \cdot (t_{IHL} + t_{ILH})}$$

CMOS oscillators can be constructed with an odd number of inverters. The oscillator frequency f_{osc} is determined by inverter low-high/high-low transitions and inverter number.


Mono-Stable Multi-Vibrator

Mono-stable multi-vibrator example constructed with NOR and inverter

 Generation of long pulse with fixed length by short trigger pulse at input


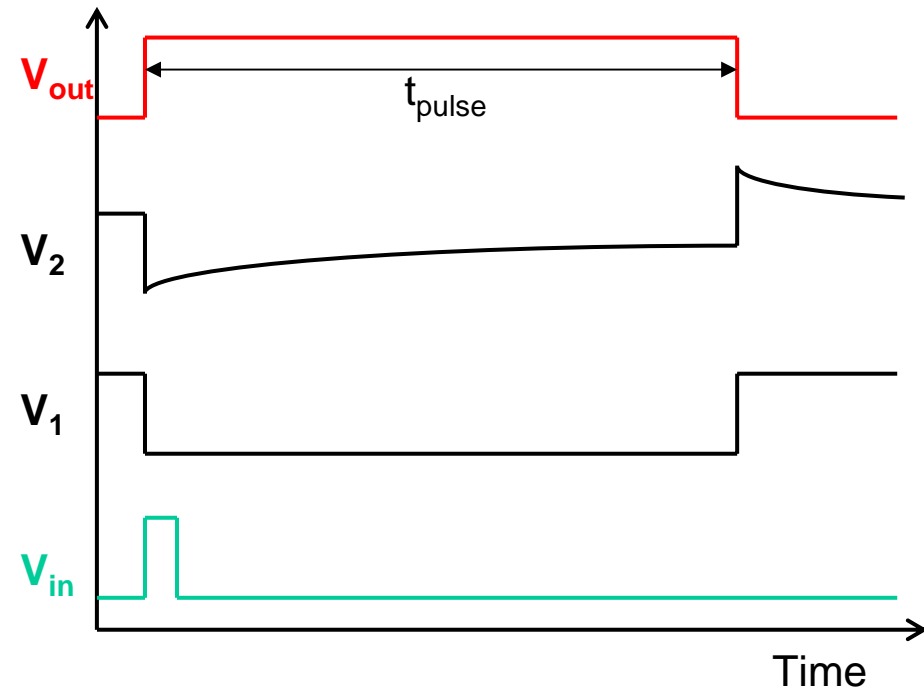
$$t_{\text{pulse}} \approx RC \cdot \ln \frac{V_{DD}}{V_{DD} - V_{SP,I}}$$




A mono-stable multi-vibrator is a circuit with delayed stable feedback. Thus pulses with fixed length can be generated.


Voltage-Generator Circuits

Simple Generator for Voltages $>V_{DD}$ and $<V_{SS}$


High-voltage generator

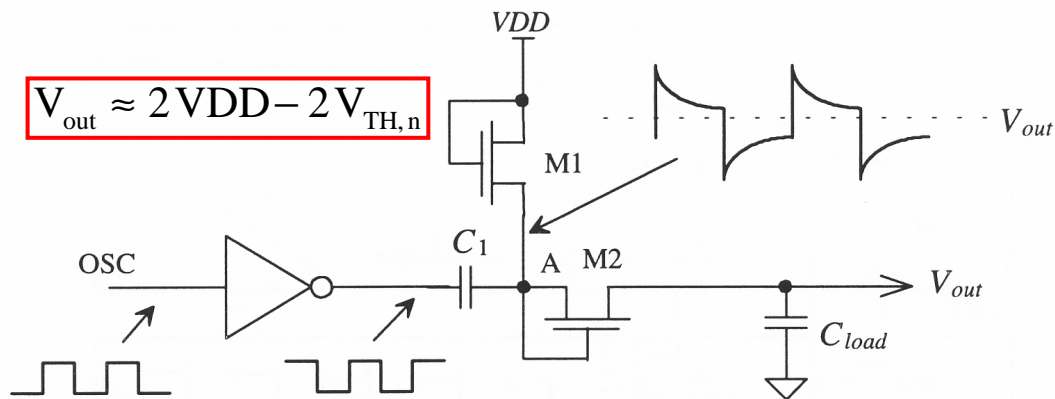

 Transient output of the high voltage generator



Low-voltage generator

 

Voltage-generator circuits are applied, if the circuits in the CMOS chip need other supply voltages than V_{DD} and V_{SS} .